
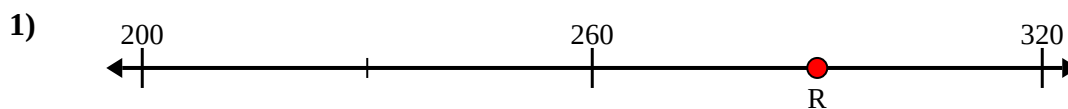


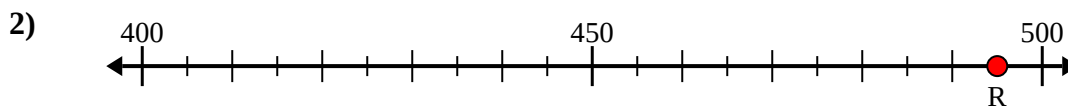


Trova il valore di R.

Risposte


1. _____




2. _____

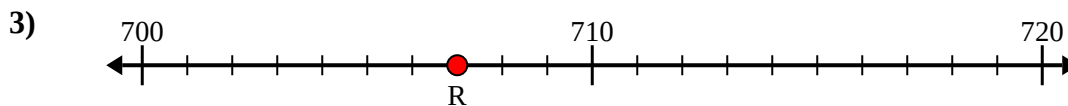


3. _____

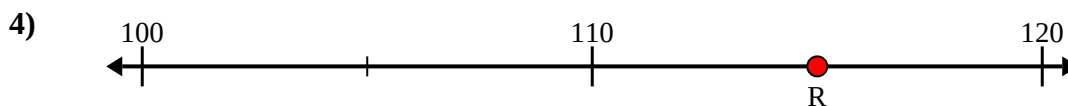


4. _____

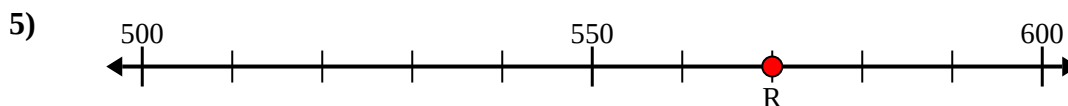


5. _____

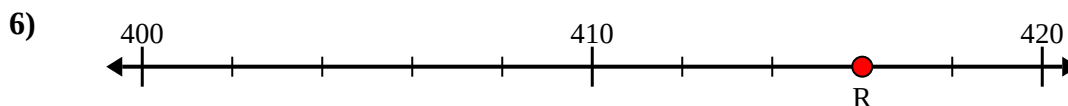


6. _____

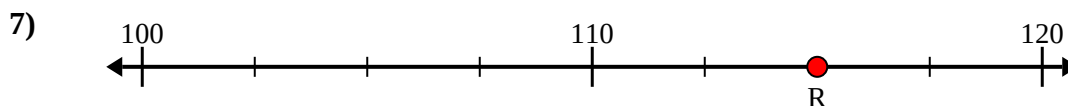


7. _____

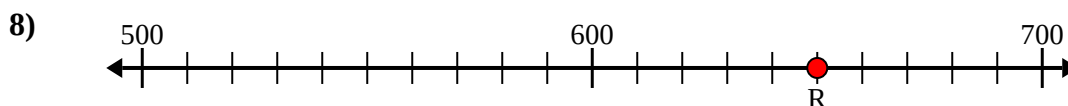

8. _____

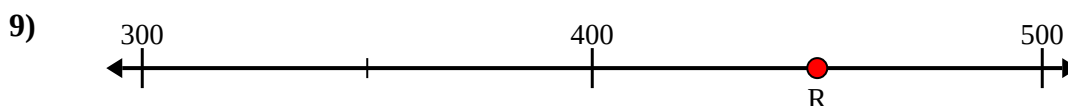











9. _____

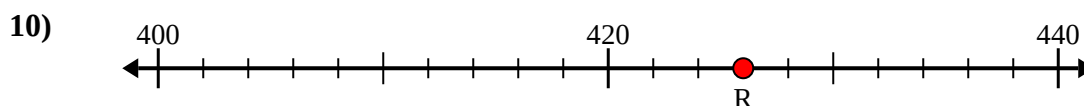

10. _____



Trova il valore di R.

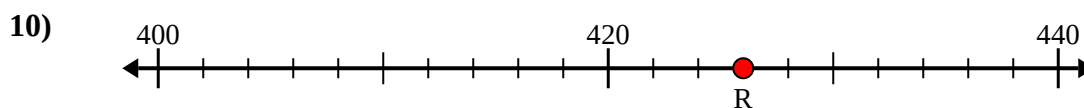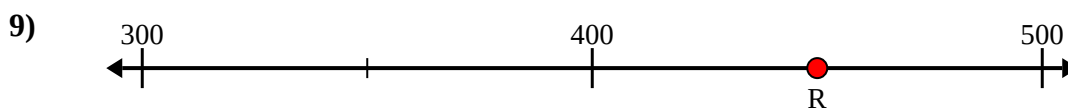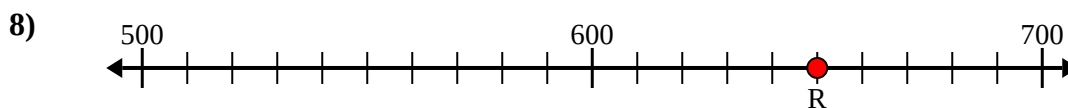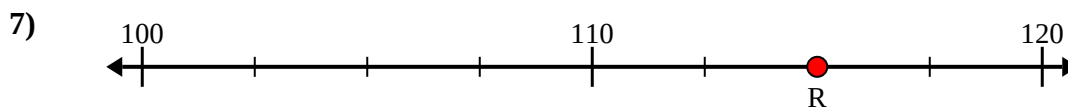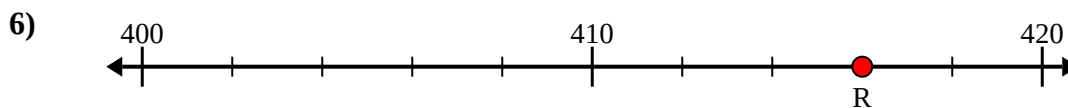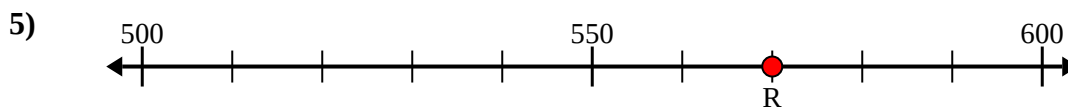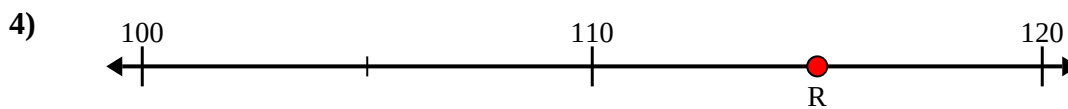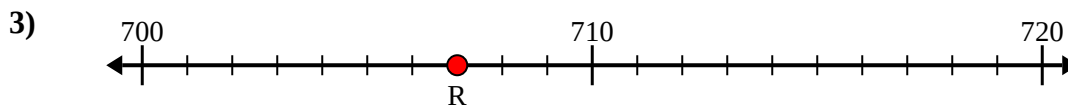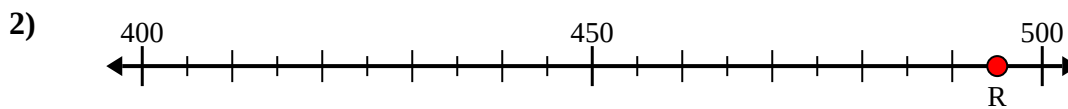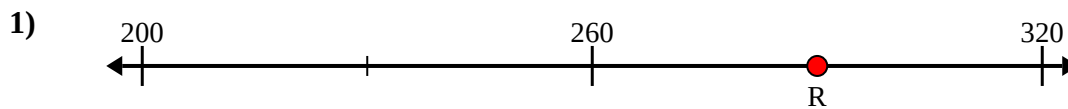**Risposte**

1. **290**
2. **495**
3. **707**
4. **115**
5. **570**
6. **416**
7. **115**
8. **650**
9. **450**
10. **426**