
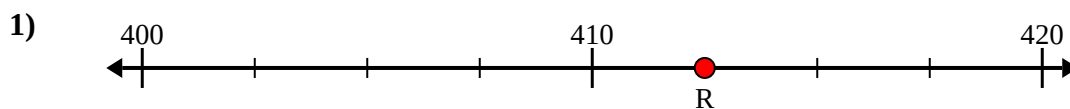


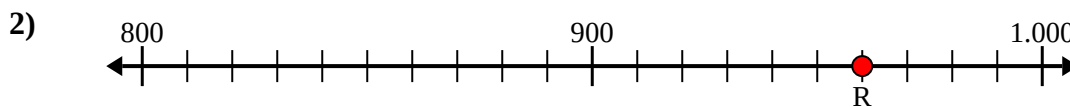


Trova il valore di R.

Risposte


1. _____




2. _____

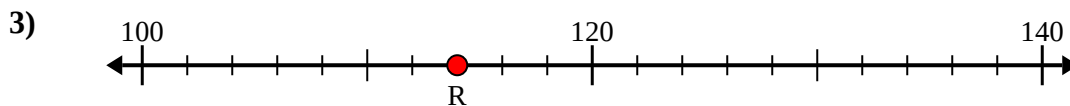


3. _____

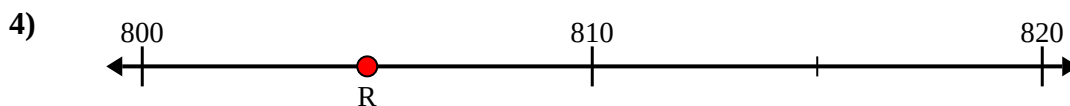


4. _____

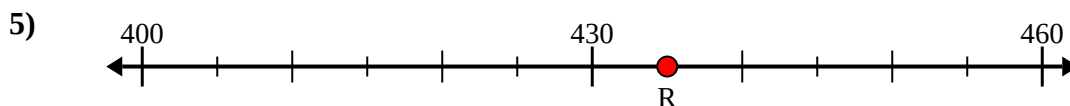


5. _____

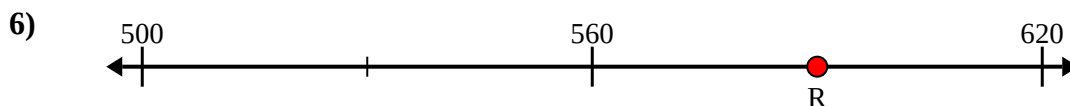


6. _____

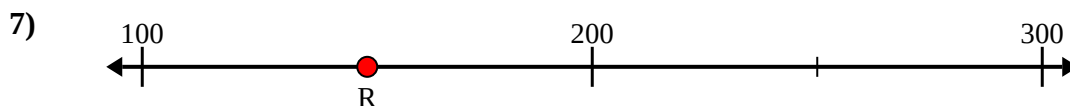


7. _____

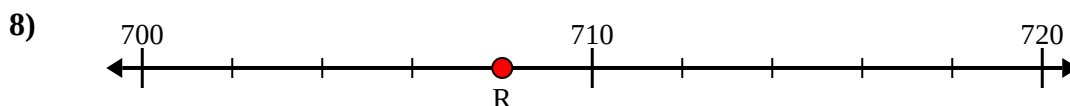

8. _____

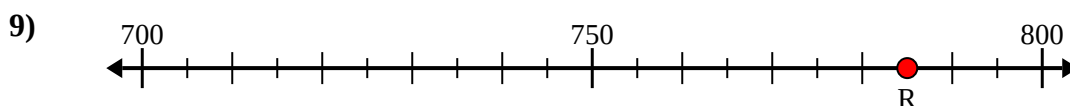










9. _____

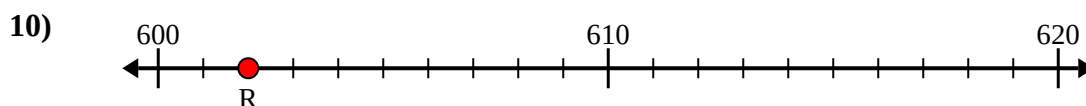

10. _____



Trova il valore di R.

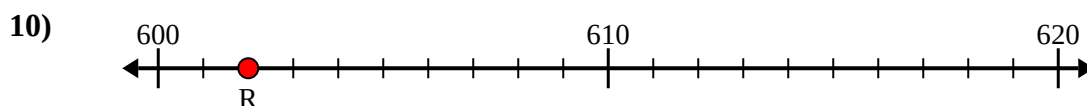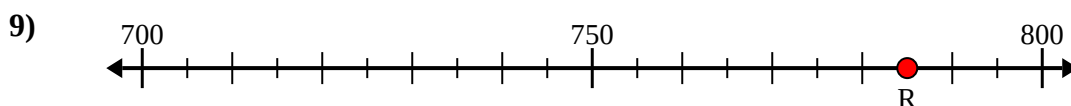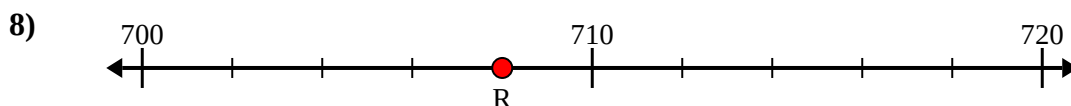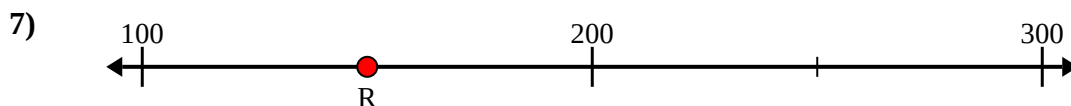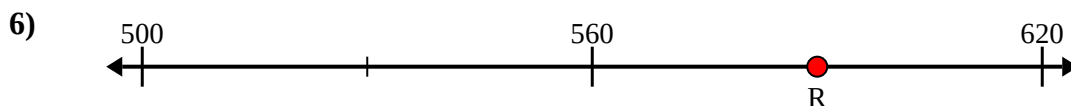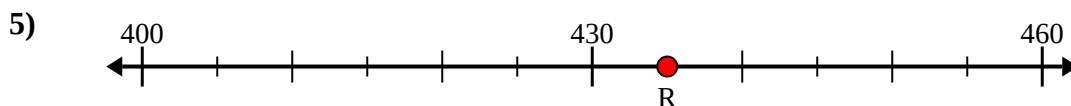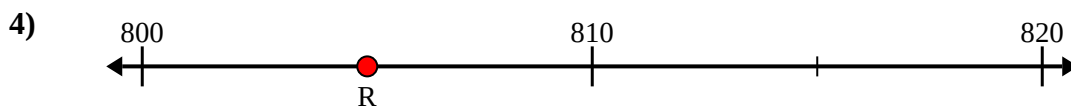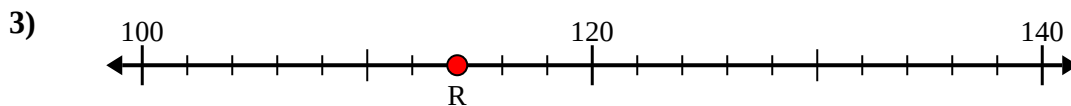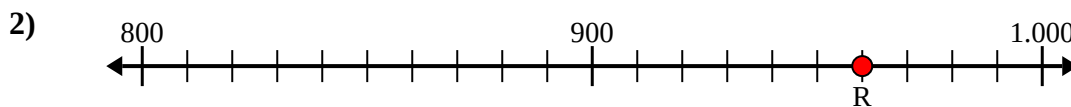**Risposte**1. **412,5**2. **960**3. **114**4. **805**5. **435**6. **590**7. **150**8. **708**9. **785**10. **602**